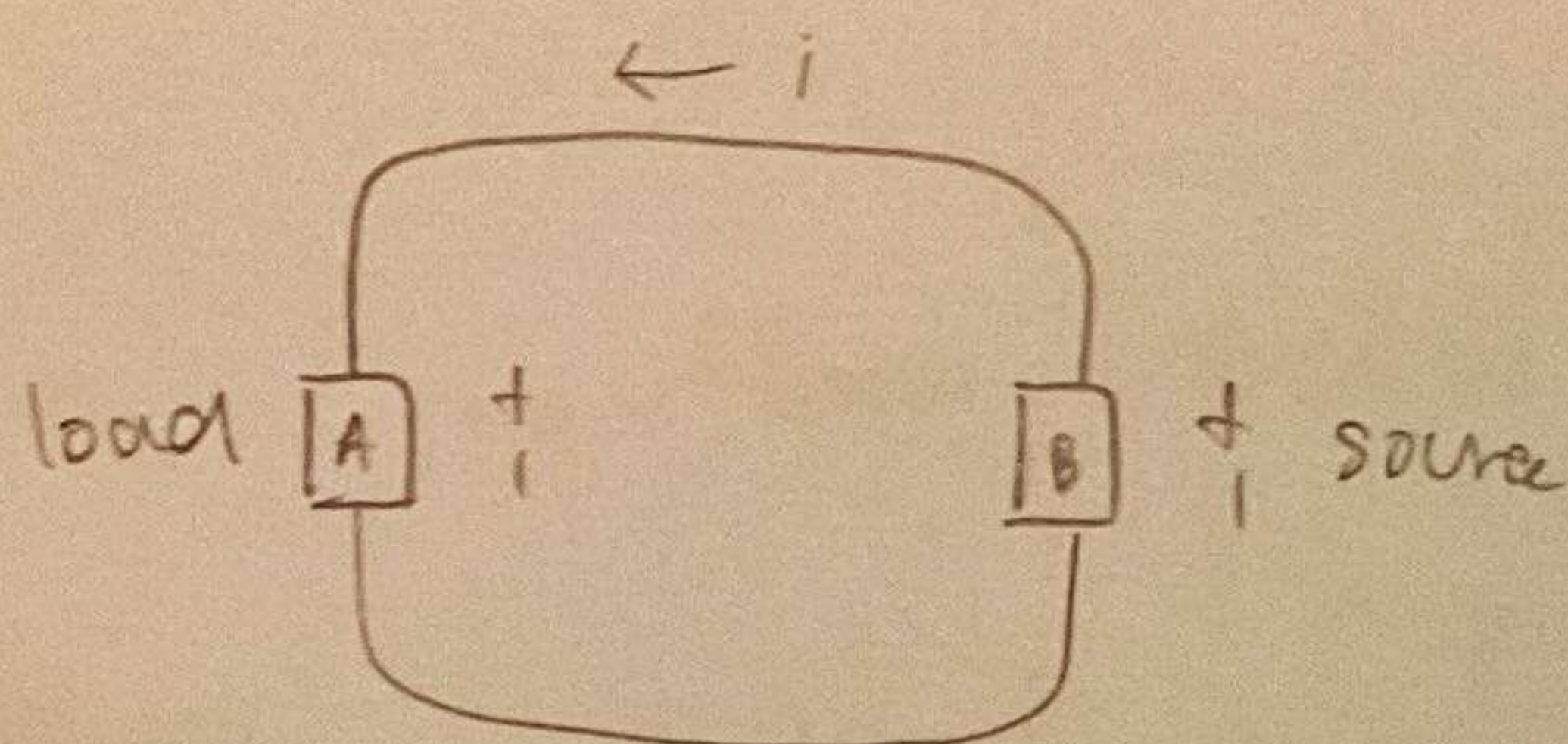


1.

a)



(Car A.)

b).

p = the rate at which electricity = $VI = 12(30) = 360 \text{ J/s}$
is used or transfer

$$\text{Energy} = \text{power} \times \text{time} = 360 \times 60 = 21600 \text{ J.}$$

2.

$$i = 15te^{-500t} \quad t \geq 0$$

$$V = 80,000te^{-500t} \quad t \geq 0$$

$$\begin{aligned} p &= 15te^{-500t} \times 80,000te^{-500t} \\ &= 12 \times 10^5 t^2 e^{-1000t} \\ &= 12 \times 10^5 t^2 e^{-1000t} \end{aligned}$$

$$\begin{aligned} \text{a). } p &= VI \\ \frac{dp}{dt} &= 12 \times 10^5 (2te^{-1000t} + t^2 e^{-1000t} (-1000)) \\ &= 24 \times 10^5 (te^{-1000t} - t^2 e^{-1000t}) = 0 \end{aligned}$$

$$t = 0; t \geq 0 \quad t < 0 \quad p = 0$$

c)

$$t = \frac{1}{500} = \frac{2}{1000} = 0.002 \text{ sec.}$$

$$\begin{aligned} p(2 \times 10^{-3}) &= 12 \times 10^5 \times (2 \times 10^{-3})^2 (e^{-1000(2 \times 10^{-3})}) \\ &= 98 \times 10^{-1} (e^{-2}) = \frac{48}{10e^2} = 0.65 \text{ Watts} \end{aligned}$$

3. absorbed

(a) $P = - (1)(2) = -2 \text{ watt}$

$5000 \times 10^{-3} = 0.5$



(b) $p(t) = 8e^{-t} \times 10^{-3} \times (1/6)(e^{-t}) = -128 \times 10^{-3} (e^{-2t}) = -0.128 (e^{-2t})$

$p(0.5) = p(\frac{1}{2}) = -0.128 (e^{-2 \times 0.5}) = -0.128 e^{-1} = -\frac{0.128}{e} = -0.049 \text{ w.}$

(c)

$P = -2(10^{-3} i_1) = -2 \times 10^{-3} (100 \times 10^{-3}) = -2 \times 10^{-4} \text{ w.}$

4.

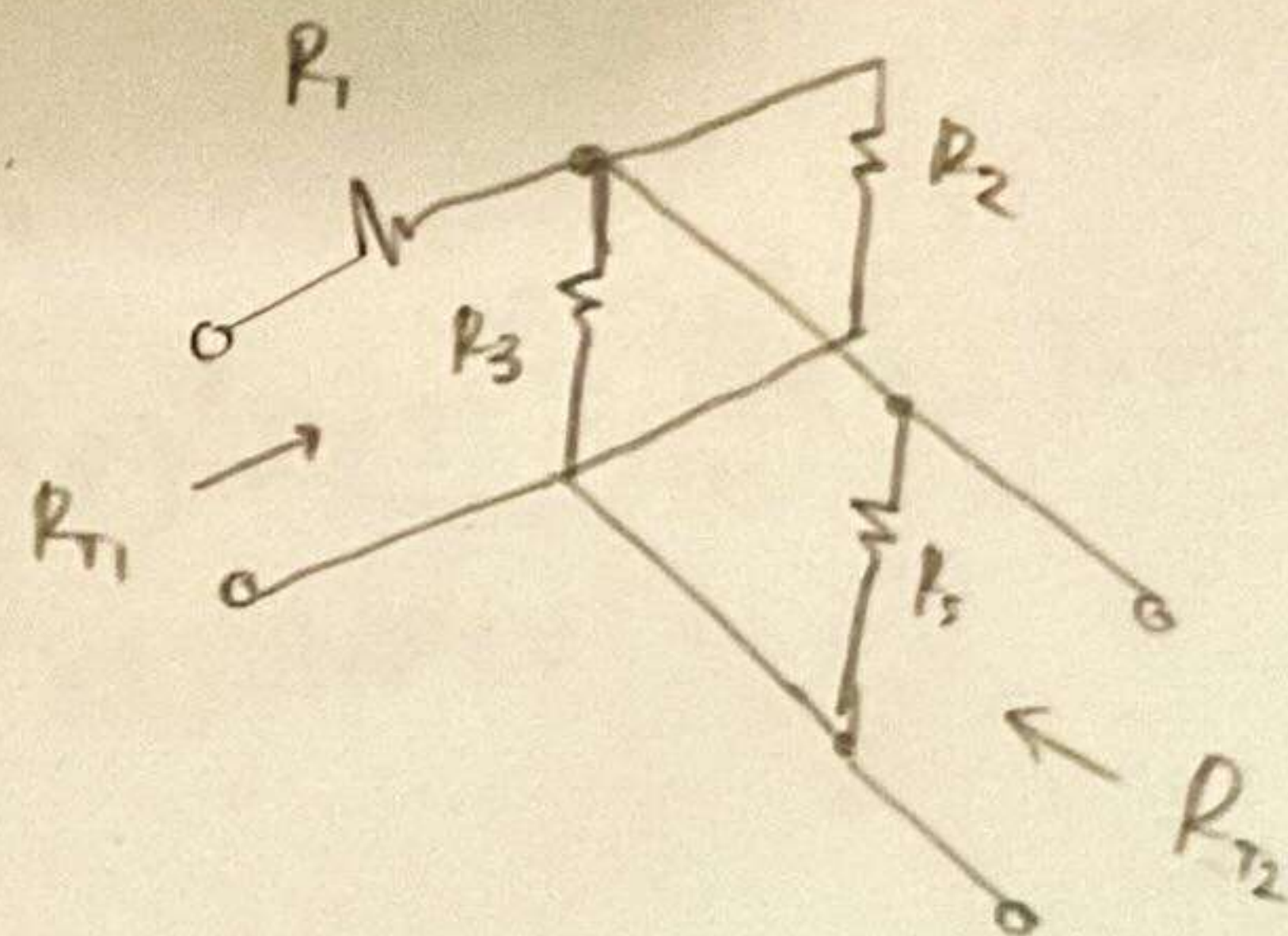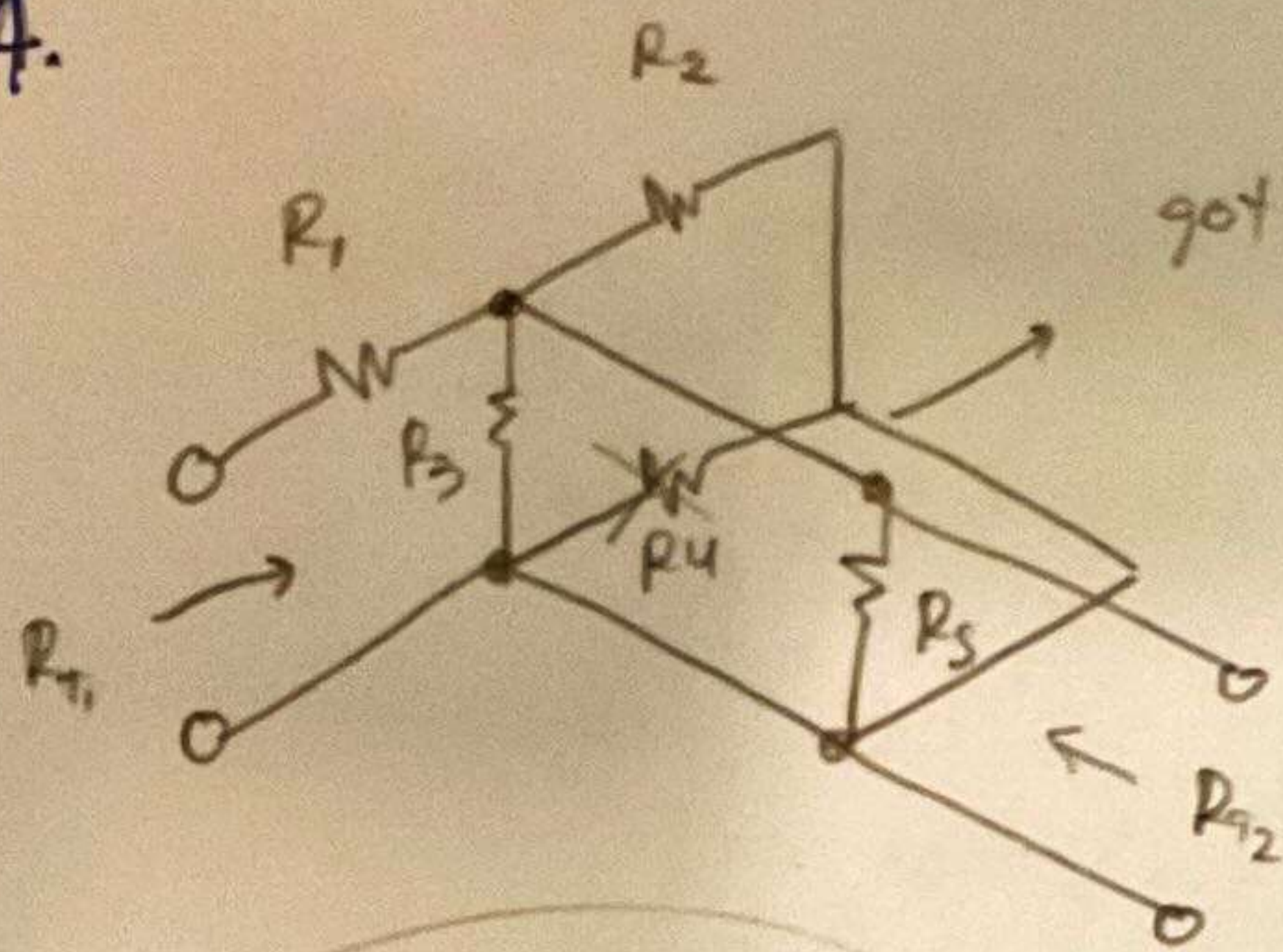



$R_{11} = R_1 + (R_3 // R_2 // R_5)$

$R_{12} = R_3 // R_2 // R_5$


5.

$$i = \frac{d}{dt} q(t)$$

$i(t)$ (mA)

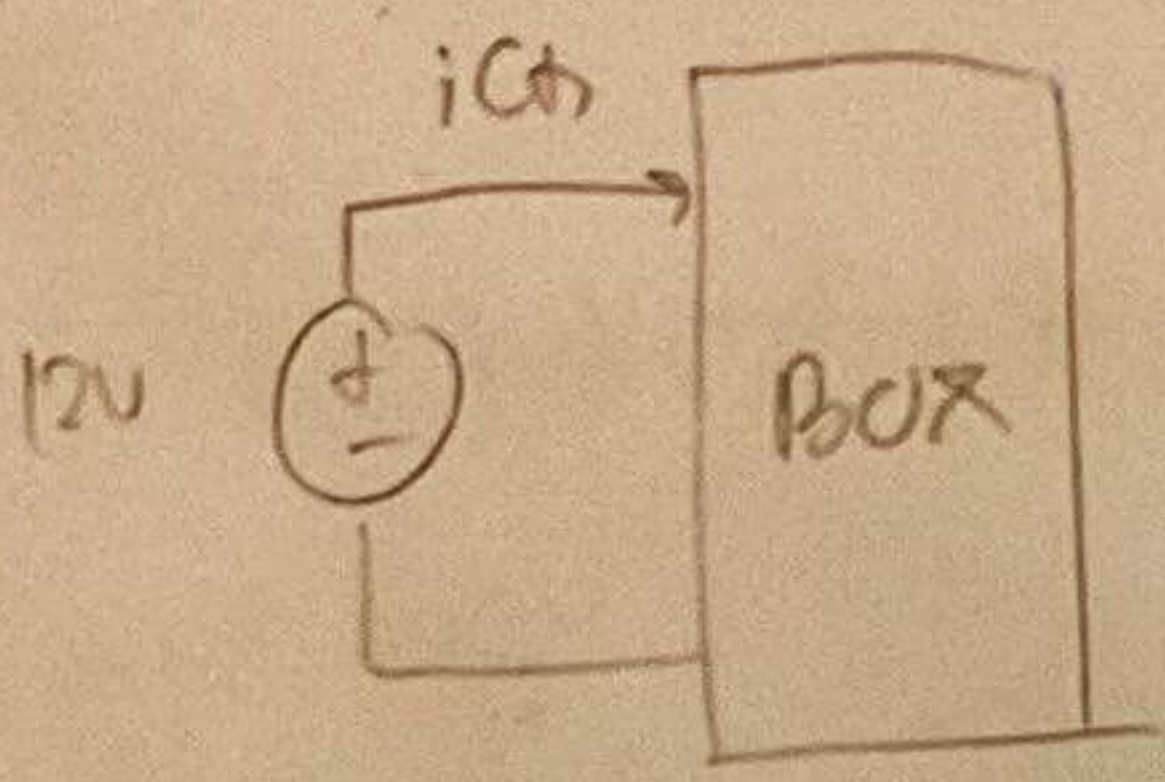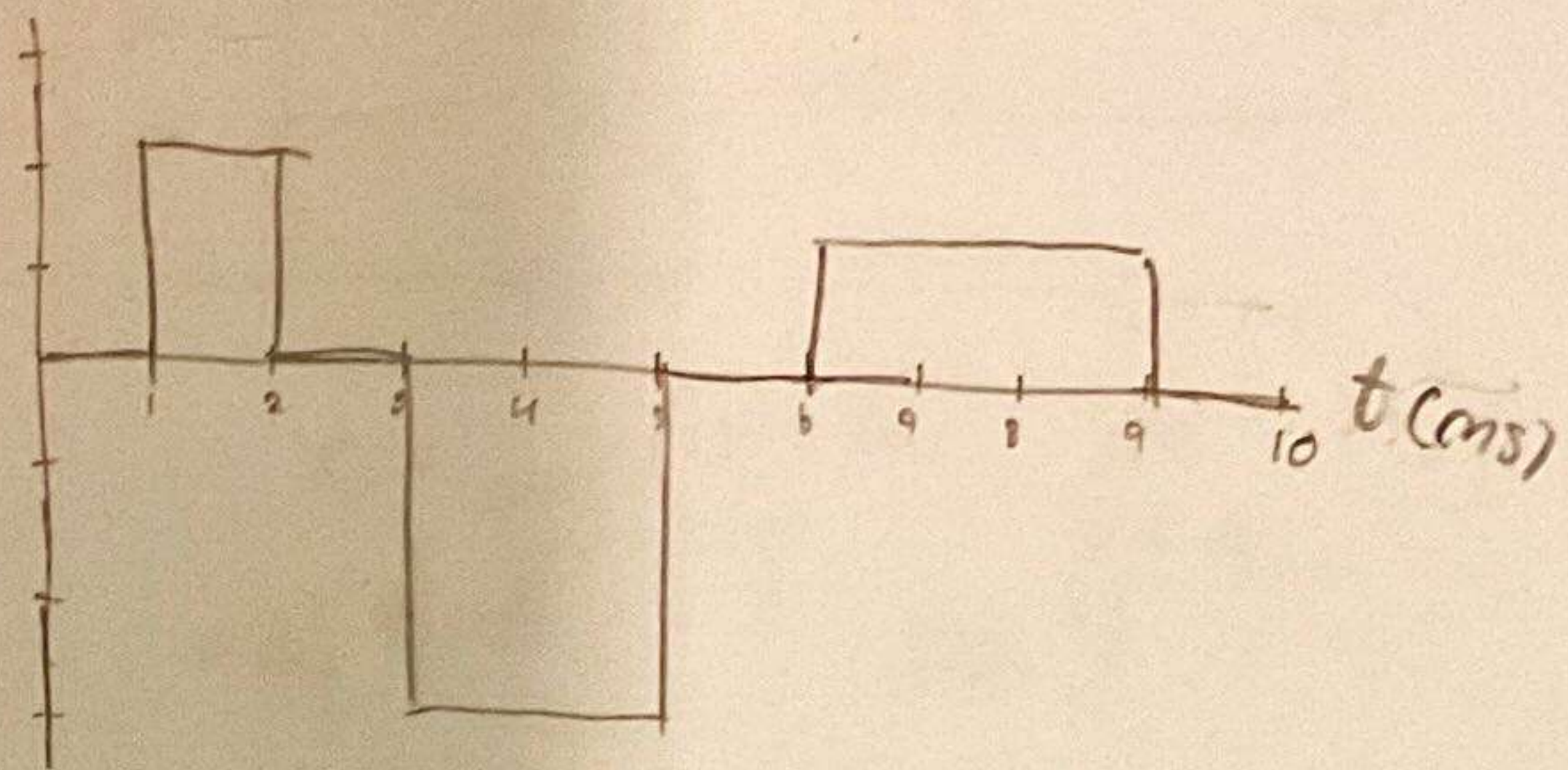

6.

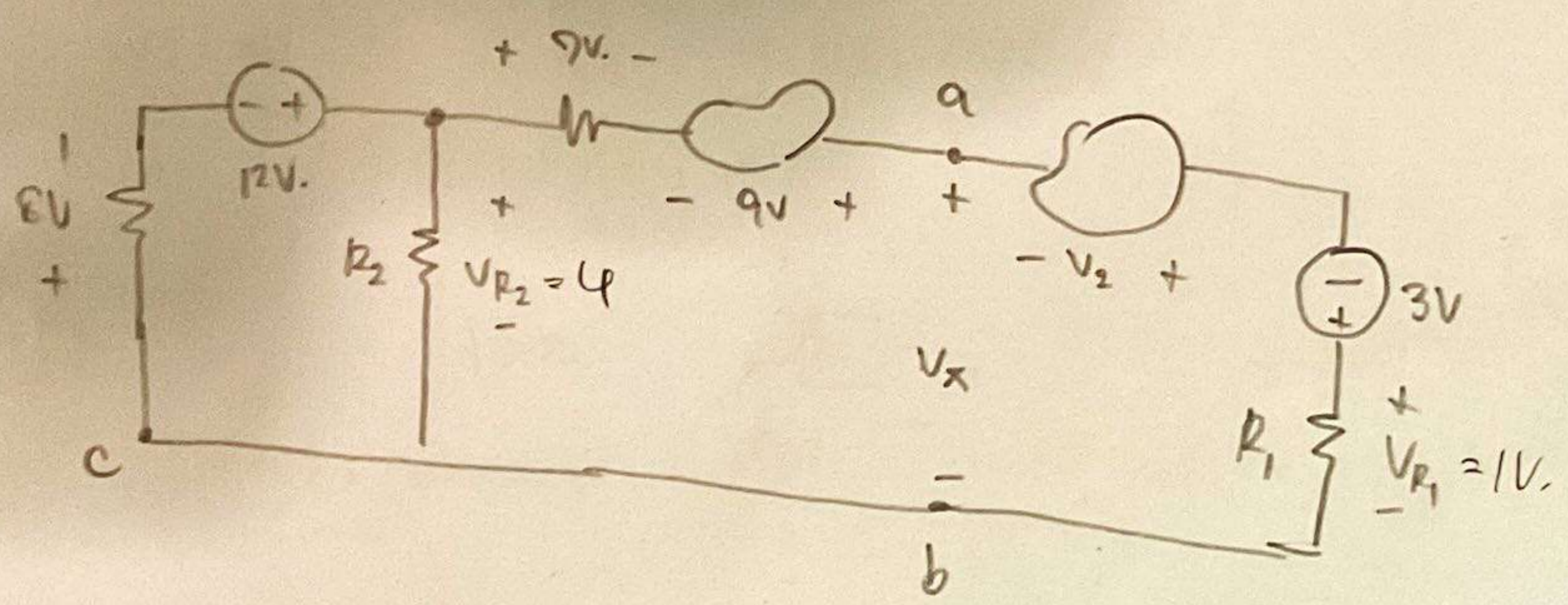

Find V_{R2} & V_2

left most loop C :

$$8 - 12 + V_{R2} = 0$$

$$V_{R2} = 4 \text{ volt} = 4V$$


right most loop C :

$$-9 + 9 - 9 - V_2 - 3 + 1 = 0$$


$$-V_2 - 8 = 0$$

$$V_2 = -8V$$

7.

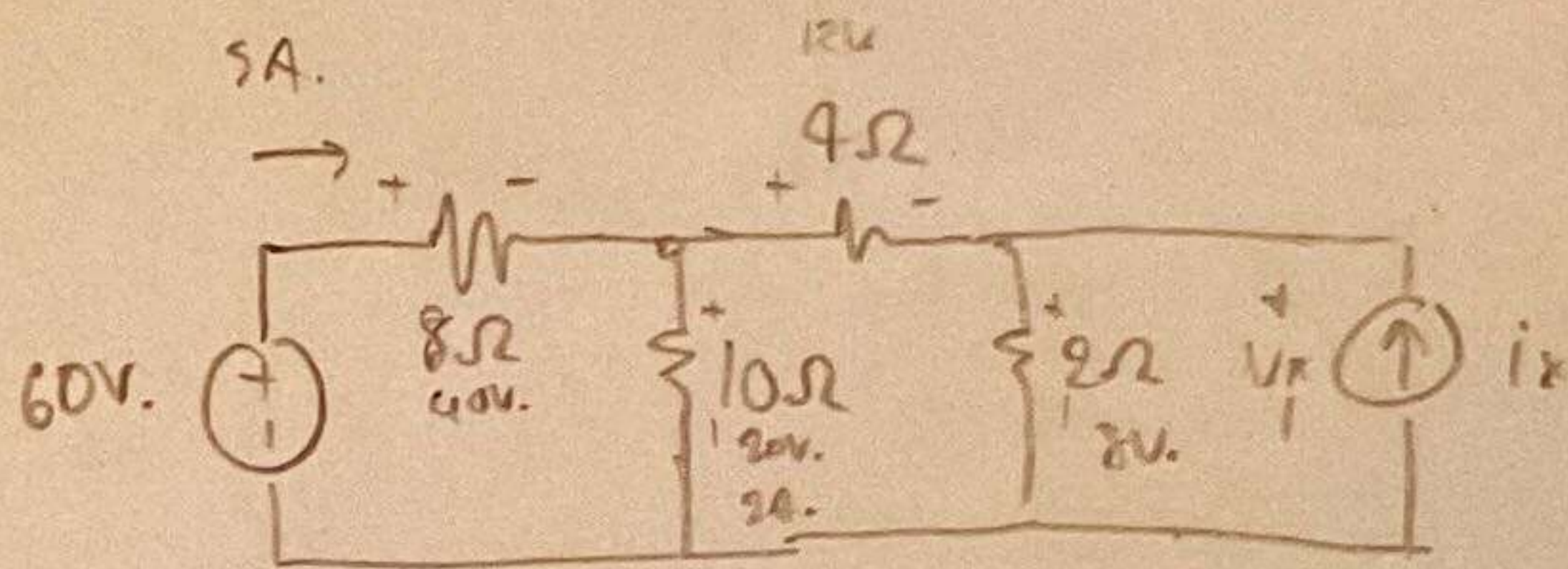

$V_x = ?$

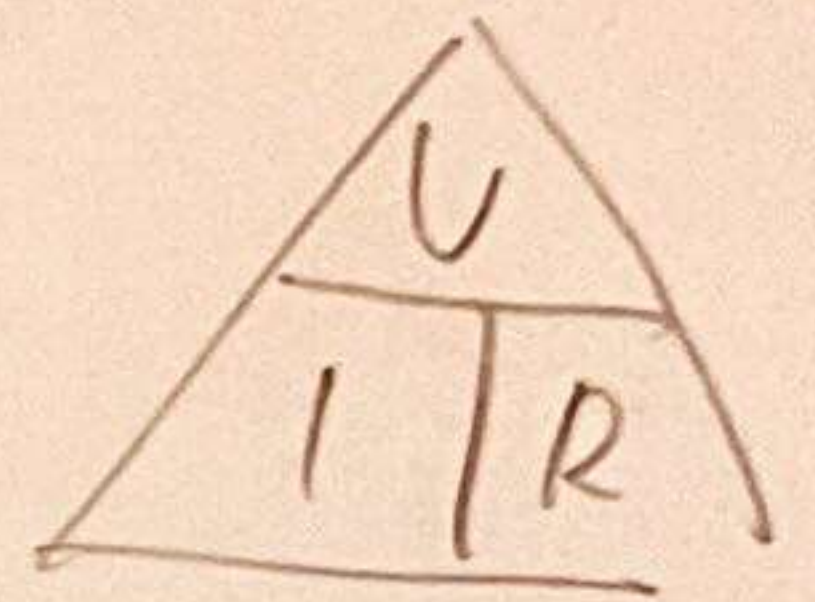






\square KVL $-60 + 40 + V_{10\Omega} = 0$
 $\frac{20}{10} = 2A$
 $V_{10\Omega} = 20V$

\square KVL $-20 + 12 + V_{2\Omega} = 0$
 $V_{2\Omega} = 20 - 12 = 8V$

\top KCL $5 - 2 - \frac{V_{4\Omega}}{4} = 0$
 $V_{4\Omega} = 3(4) = 12V$

\square KCL $-8 + V_x = 0$
 $V_x = 8V$

8.

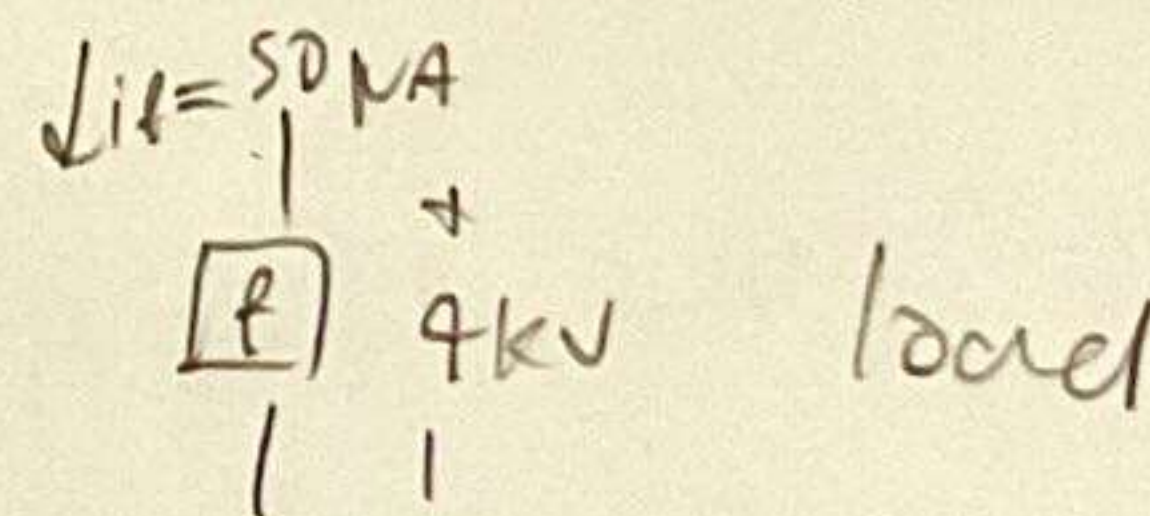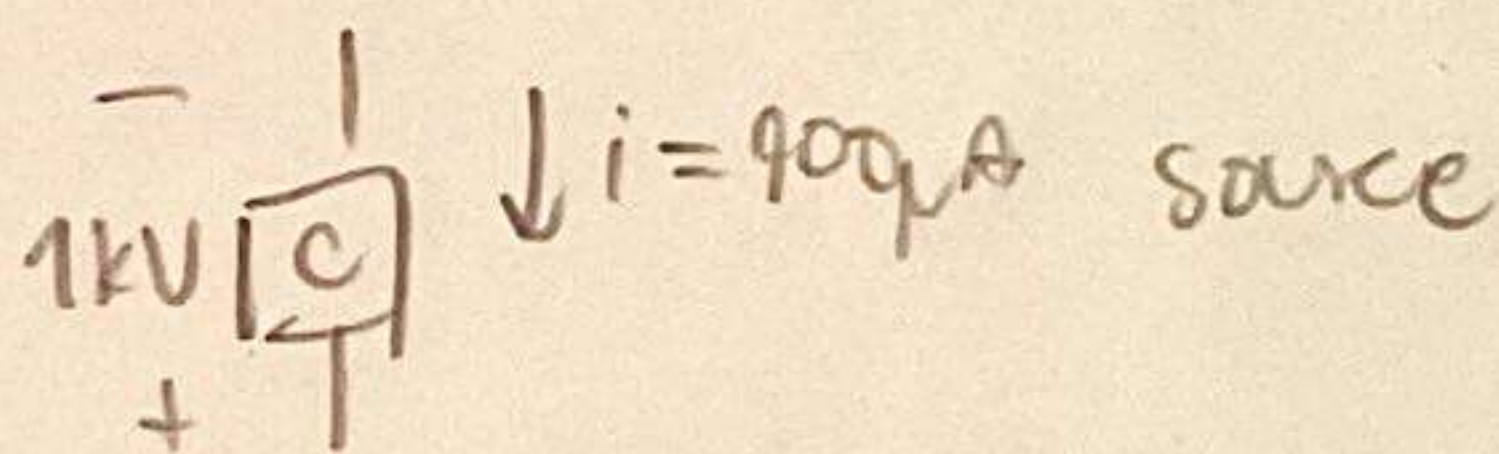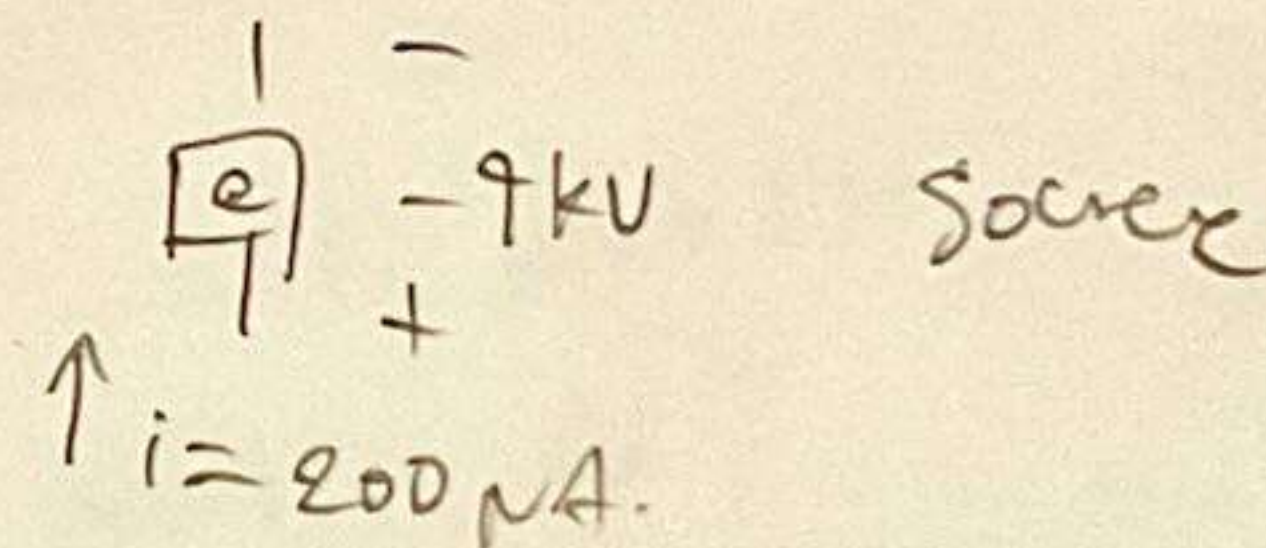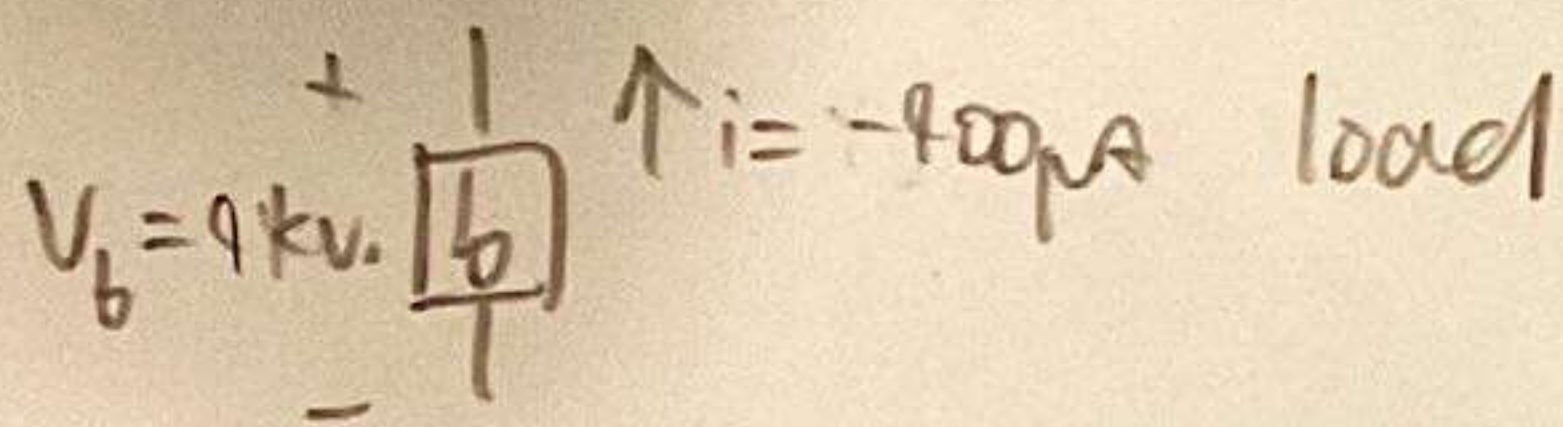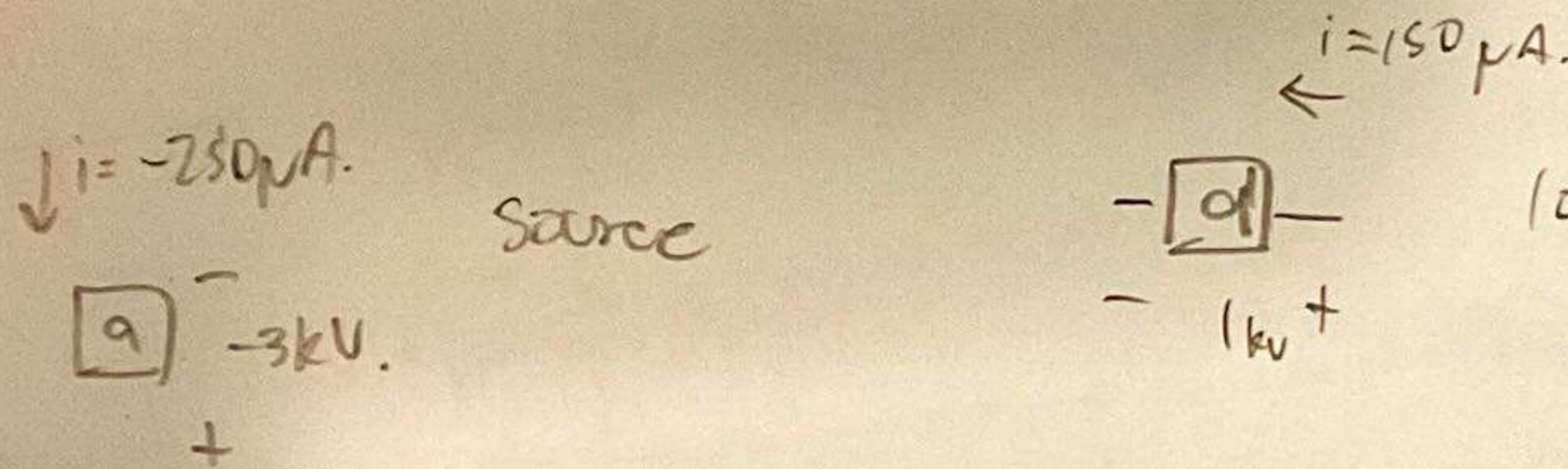


a source b load c source d load e source f load

$(-250 \times 3) + (4 \times 400) + (-1 \times 400) + (1 \times 150) + (-9 \times 200) + (4 \times 50) = 0$

$= 0$

Use Tellegen's theorem

9.

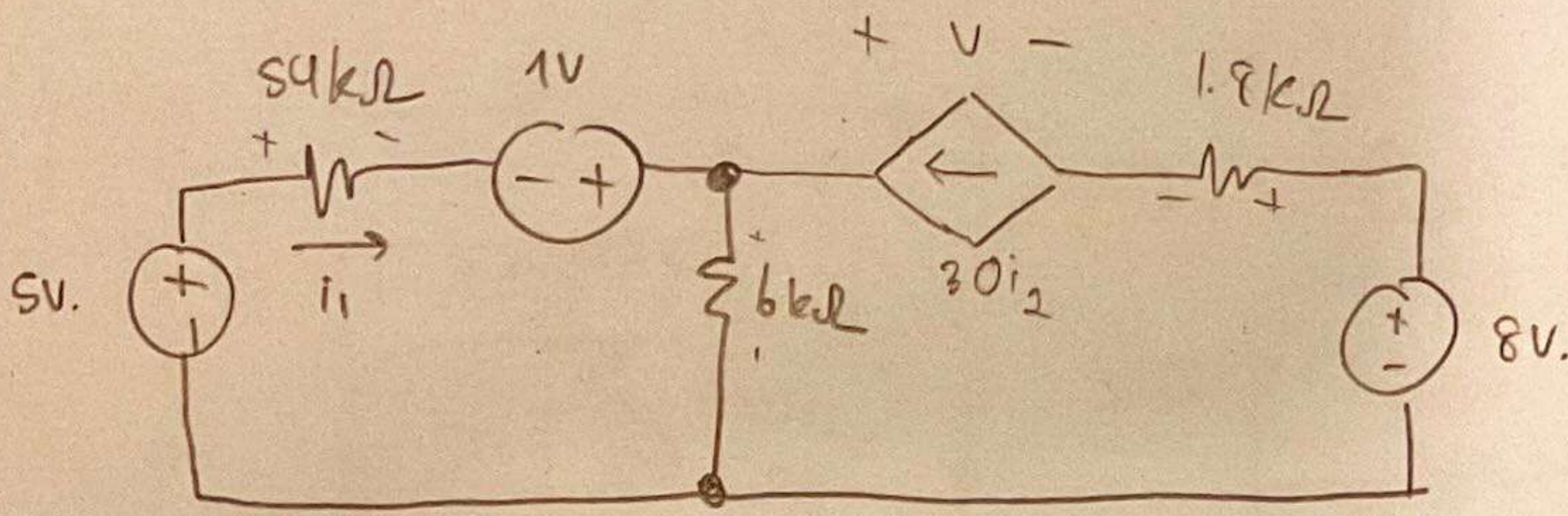


$I = \text{mA}$

$V =$

$R = \text{k}\Omega$

(a) i_1 in microamperes

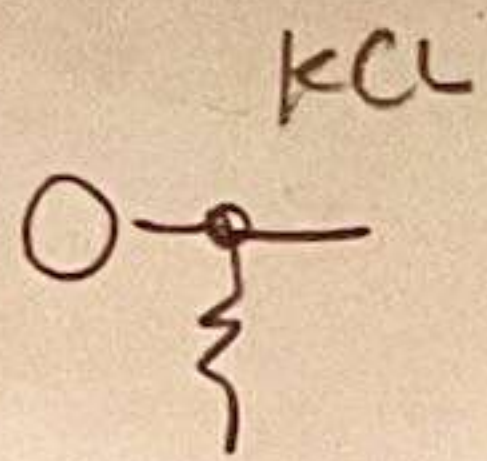


$$i_1 + 30i_1 - i_{6k} = 0$$

$$i_{6k} = 31i_1$$

$$V_{6k} = (31i_1)(6) = 186i_1$$

$$V_{54k} = i_1 54$$

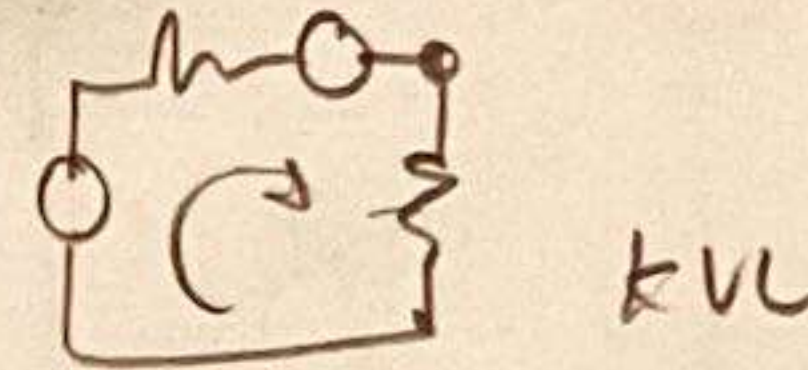

$$-54i_1 - 1 + 186i_1 + 8 = 0$$

$$240i_1 = 6$$

$$i_1 = \frac{6}{240} = \frac{1}{40}$$

$$i_1 = 0.025$$

$$i_1 = 25 \mu\text{A} \quad (a)$$

$$= 25 \times 10^{-6}$$



$$-54 + (0.025)(54) - 1 + V - 1.8(30)(0.025) + 8 = 0$$

$$V = -2 \text{ Volts} \quad (b)$$

(c) total power generated

$$P = 5(0.025) + 1(0.025) + 8(30)(0.025)$$

$$= 6.15 \text{ mW} = 6150 \text{ W}$$

(d) total power absorb

$$P = (0.025)^2(54) + 186(0.025)(31) + (2)(30)(0.025) + 1.8(30)^2(0.025)^2$$

$$= 6.15 \text{ mW} = 6150 \text{ W}$$




or use Tellegen Theorem

$$\text{power absorb} + \text{power generate} = 0$$

$$\text{power absorb} = \text{power generate}$$

-2 + This dependent current source, after calculation seems to absorb power.

10.

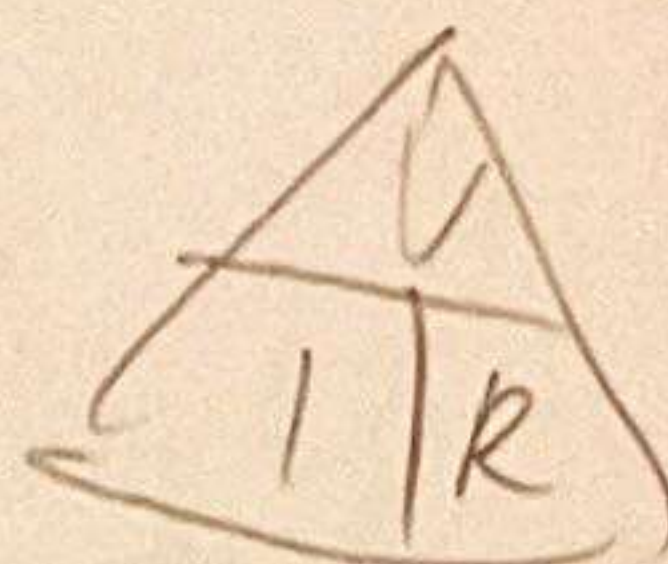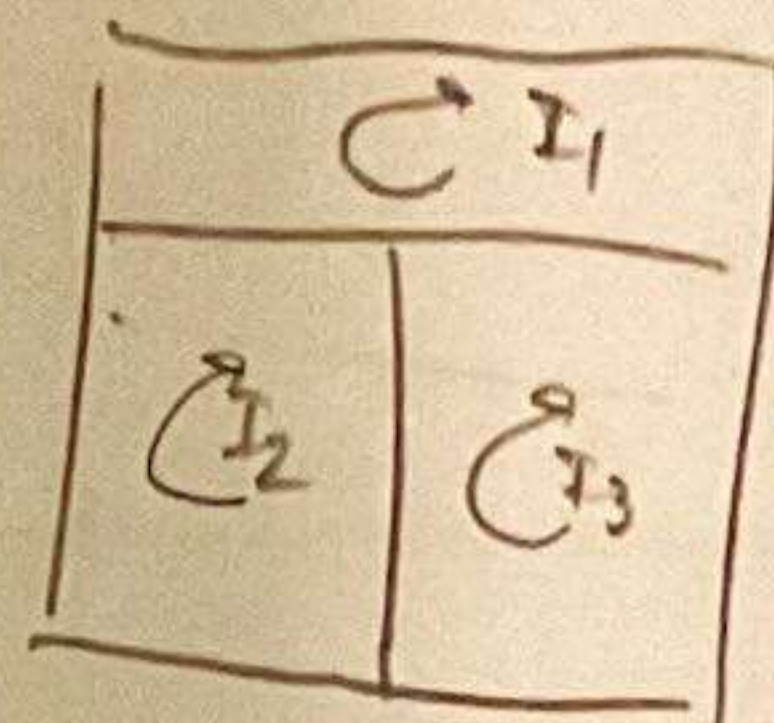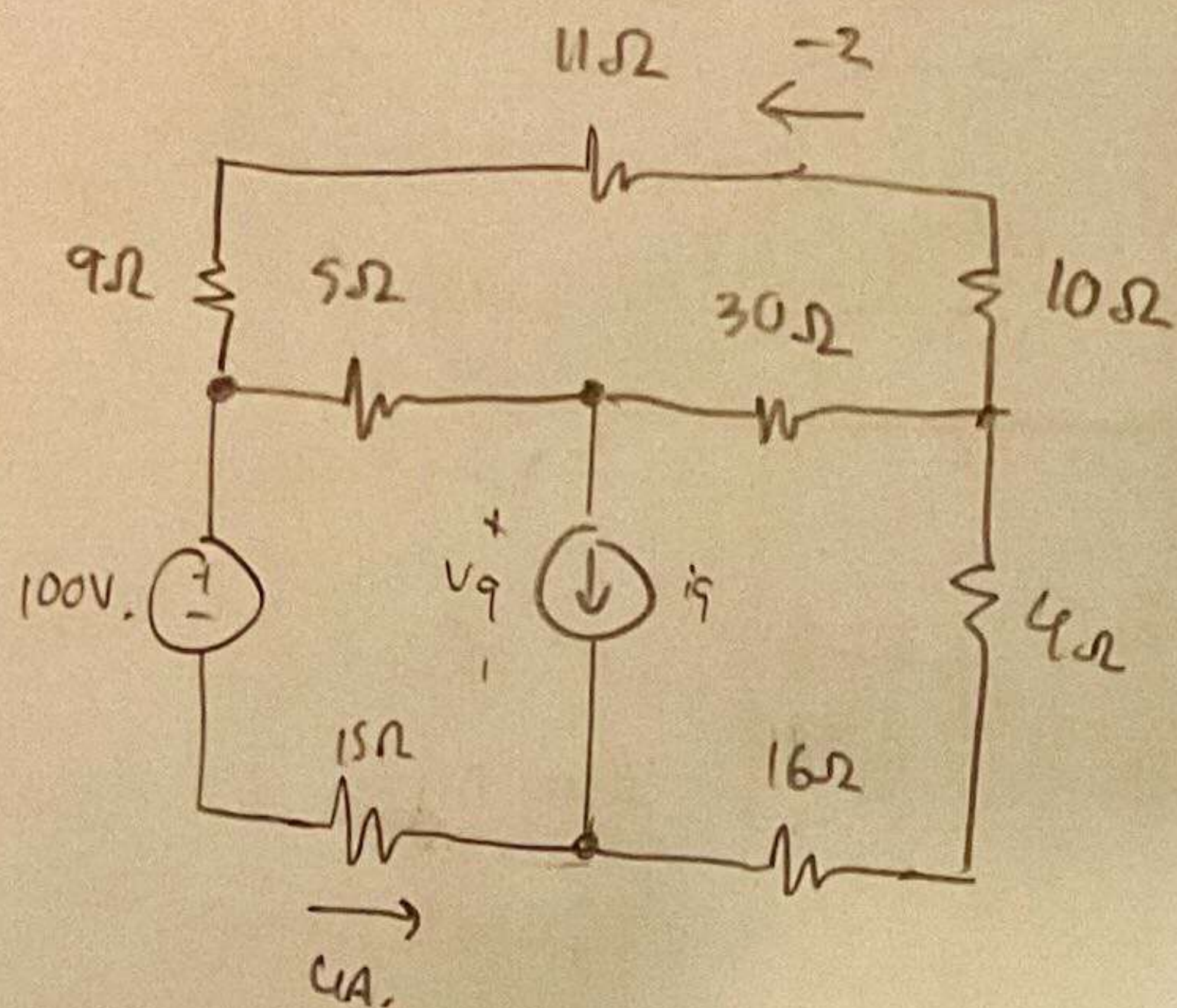

$$I_2 - I_3 = i_g \quad (1)$$

Supermesh ($I_2 + I_3$) \rightarrow

$$I_2 = -4$$

$$I_1 = 2$$

$$I_3 = 5$$


$$\begin{aligned} 15(I_2) - 100 + 5(I_2 - I_1) + (I_3 - I_1)(30) + 4I_3 + 16I_3 &= 0 \\ -60 - 100 + 5(-6) + (I_3 - 2)(30) + 4I_3 + 16I_3 &= 0 \\ -60 - 100 - 30 + 30I_3 - 60 + 4I_3 + 16I_3 &= 0 \end{aligned}$$

$$50I_3 = 250$$

$$I_3 = 5$$

$$(1): -9 - 5 = -4A = I_g \quad (a)$$


(c)

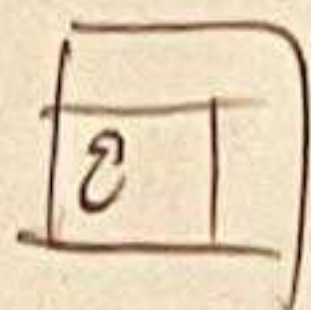

$$-4(1) - 100 + 5(-6) + V_g = 0$$

$$V_g = 190 \quad (c)$$

(b)

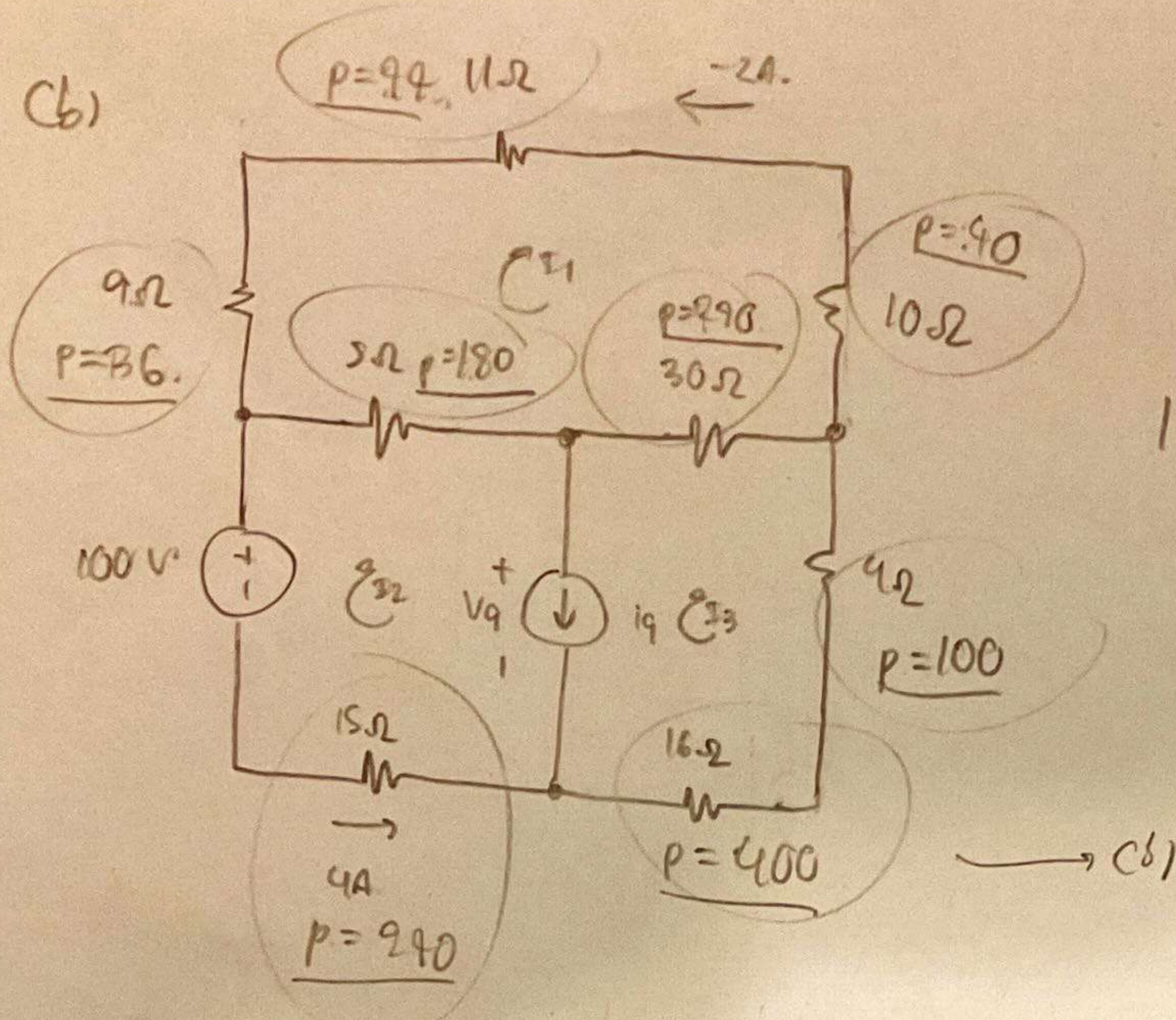

$$(I_2 - I_1)(5) = 180$$

$$(I_3 - I_1)(30) = 270$$

This one is a
LOAD not a
source.



(c)

$$36 + 44 + 40 + 270 + 180 + 100 + 400 + 240 + 400 = 1910 \rightarrow \text{absorbed}$$

$$-9(190) = -1910 \rightarrow \text{generated}$$

$$\text{absorbed} + \text{generated} = 0 = 1910 - 1910 = 0$$