

(8 marks) Q5B A DAC is used to control the speed of a motor. The 0 to 4 mA analog current from the DAC is amplified to produce motor speed from 0 to 2000 rpm. **Explain** how many bits should be used to produce a motor speed that is within 1 rpm of the desired speed?

$$\frac{2000}{1023} = 1.96$$


$$\frac{2000}{2} = 1000 \text{ steps} = 2^{10}$$

10 bits

$$\begin{array}{c} 501 \\ 500 \\ 499 \end{array} \begin{array}{c} \text{---} \\ \uparrow \\ \downarrow \\ \text{---} \end{array} \begin{array}{c} \\ 2 \text{ rpm} \\ \end{array}$$

n bits right shifters


external input

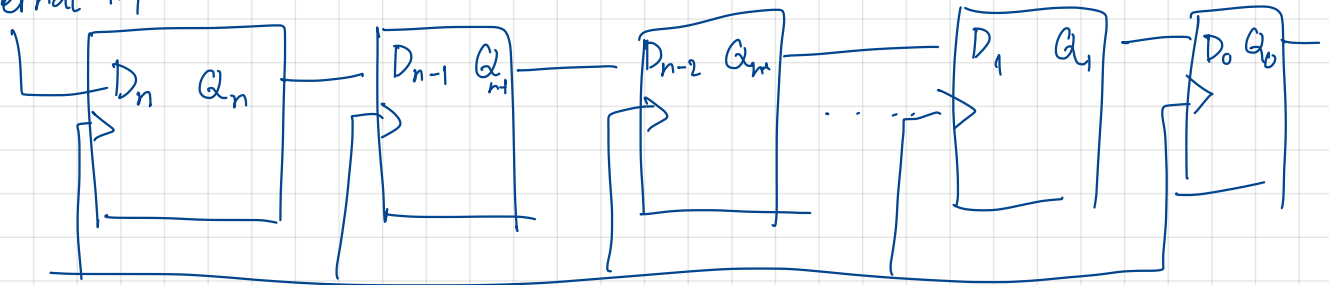


0110  
1011  
1101

n bits left shifters


external input

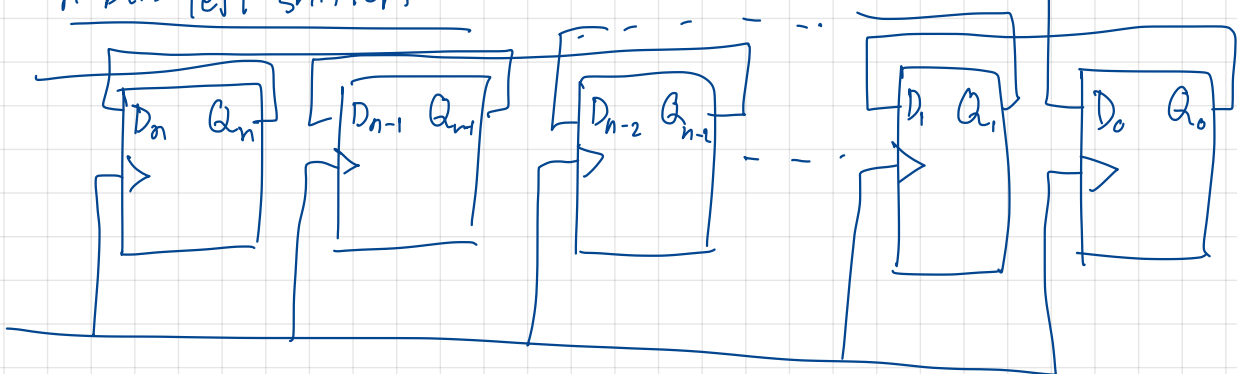

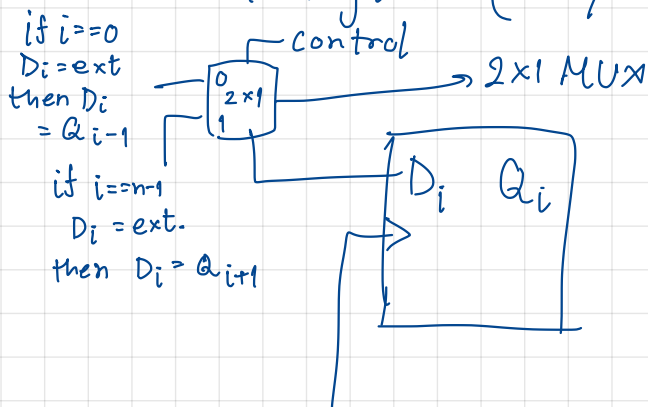Shift register (left/right)  $0 \leq i \leq n$



## MOD 6 synchronous counter using JK

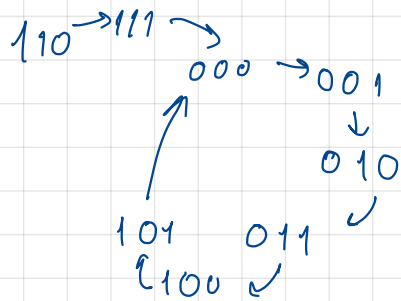

	J	k
0 → 0	0	x
0 → 1	1	x
1 → 0	x	1
1 → 1	x	0

PS			NS			$J_c k_c$		$J_b k_b$		$J_a k_a$	
C	B	A	C	B	A	$J_c$	$k_c$	$J_b$	$k_b$	$J_a$	$k_a$
0	0	0	0	0	1	0	x	0	x	1	x
0	0	1	0	1	0	0	x	1	x	x	1
0	1	0	0	1	1	0	x	x	0	1	x
0	1	1	1	0	0	1	x	x	1	x	1
1	0	0	1	0	1	x	0	0	x	1	x
1	0	1	0	0	0	x	1	0	x	x	1
1	1	0	1	1	1	x	0	x	0	1	x
1	1	1	0	0	0	x	1	x	1	x	1

$$J_A = 1$$

$$K_A = 1$$

$$J_B = \bar{C}A$$

$$K_B = A$$

$$J_C = BA$$

$$K_C = A$$


$J_B$

BA	00	01	11	10
0	0	1	x	x
1	0	0	x	x

$K_C$

BA	00	01	11	10
0	x	x	x	x
1	0	1	1	0

## MOD -5 synchronous counter using JK

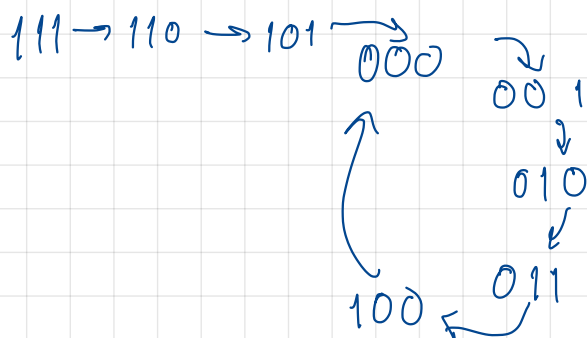

excitation table

	J	k
0 → 0	0	x
0 → 1	1	x
1 → 0	x	1
1 → 1	x	0

PS			NS			$J_c k_c$		$J_b k_b$		$J_a k_a$	
C	B	A	C	B	A	$J_c$	$k_c$	$J_b$	$k_b$	$J_a$	$k_a$
0	0	0	0	0	1	0	x	0	x	1	x
0	0	1	0	1	0	0	x	1	x	x	1
0	1	0	0	1	1	0	x	x	0	1	x
0	1	1	1	0	0	1	x	x	1	x	1
1	0	0	0	0	0	x	1	0	x	0	x
1	0	1	0	0	0	x	1	0	x	0	x
1	1	0	1	0	1	x	0	x	1	1	x
1	1	1	1	1	0	x	0	x	0	x	1

$$K_A = 1$$

$$J_A = B + \bar{C}$$


$$K_C = \bar{B}$$

$$J_C = BA$$

$$K_B = \bar{C}A + C\bar{A}$$

$$J_B = \bar{C}A$$

$S_1$	$S_0$	
0	0	Hold
0	1	R
1	0	L
1	1	Parallel

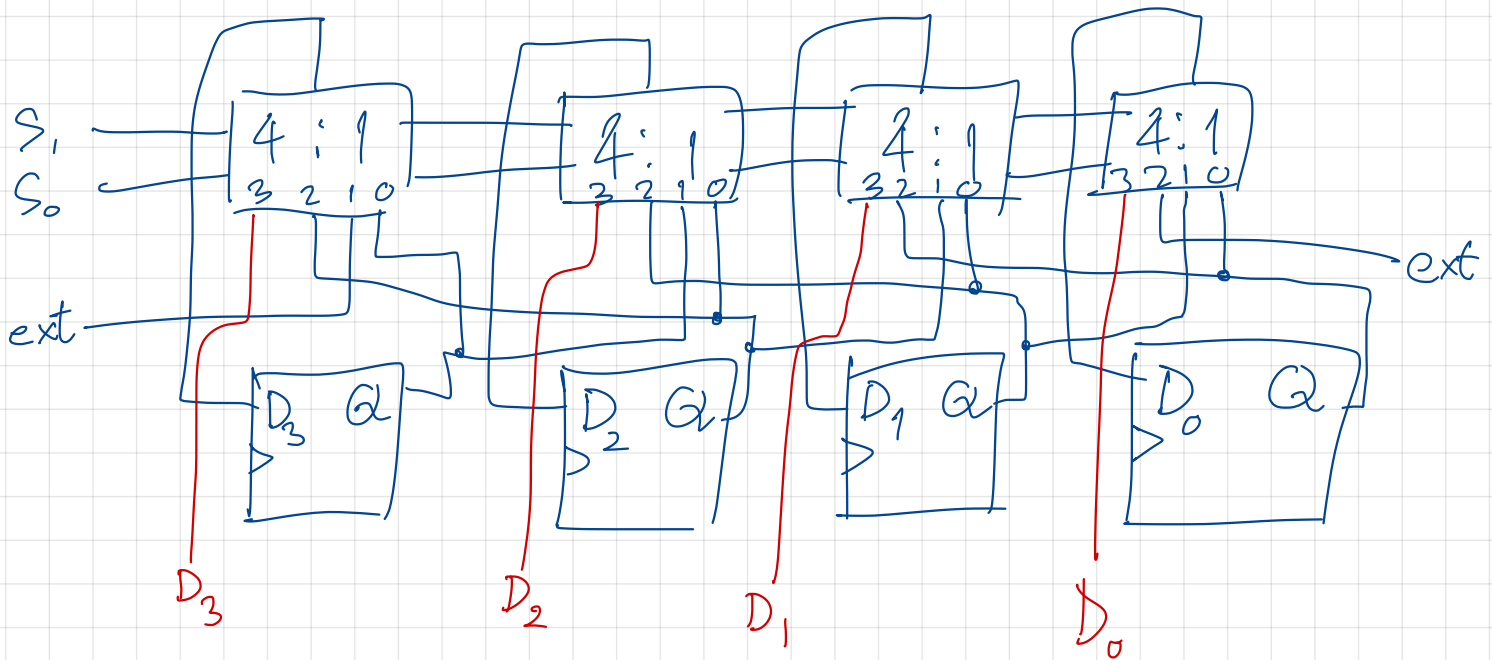

A	B	$B_{in}$	Diff	$B_{out}$
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1