

**Mahidol University, International College & Faculty of Engineering**  
**Department of Computer Engineering**  
**Final Examination**  
**EGCI 234: Digital Circuit Design (T2/2021-22)**

**WebEx Q4**

Date: 4 April 2022

Time: 2 Hours

Total Mark: 50 marks

**Instruction:** Answer all questions and submit to our Google ClassroomQuestions 1 & 2 25 minutes/ 5 & 9 marks (1000-1025) **MSI & Arithmetic Circuits**

- 5 min break -

Questions 3 15 minutes/ 3 & 5 marks (1030-1045) **Flip Flops**

- 5 min break -

Questions 4 20 minutes/ 10 marks (1050-1110) **Sequential Circuit Design**

- 5 min break -

Questions 5 20 minutes/ 4 & 8 marks (1115-1135) **ADC & DAC**

- 5 min break -

Questions 6 10 minutes/ 6 marks (1140-1150) **Digital Circuit Design****Explanation**

Examination will start at 1000. Questions 1 & 2 will be released via Google classroom. Students have 25 minutes to answer the question and submit to Google classroom before deadline (ie. 1025). Followed by 5-minute break. Then questions 2 will be released ..


$0 \rightarrow 0$     $0 \times$   
 $0 \rightarrow 1$     $1 \times$   
 $1 \rightarrow 0$     $x \ 1$   
 $1 \rightarrow 1$     $x \ 0$

**(10 marks) Sequential Circuit Design****(10 marks) Q4 Show how to design a MOD-13 synchronous up counter using JK FFs.**

PS      NS

D	C	B	A	D	C	B	A	J <sub>D</sub>	k <sub>D</sub>	J <sub>C</sub>	k <sub>C</sub>	J <sub>B</sub>	k <sub>B</sub>	J <sub>A</sub>	k <sub>A</sub>
0	0	0	0	0	0	0	1	0	x	0	x	0	x	1	x
0	0	0	1	0	0	1	0	0	x	0	x	1	x	x	1
0	0	1	0	0	0	1	1	0	x	0	x	x	0	1	x
0	0	1	1	0	1	0	0	0	x	1	x	x	1	x	1
0	1	0	0	0	1	0	1	0	x	x	0	0	x	1	x
0	1	0	1	0	1	1	0	0	x	x	0	1	x	x	1
0	1	1	0	0	1	1	1	0	x	x	0	x	0	1	x
0	1	1	1	1	0	0	0	1	x	x	1	x	1	x	1
1	0	0	0	1	0	0	1	x	0	0	x	0	x	1	x
1	0	0	1	1	0	1	0	x	0	0	x	1	x	x	1
1	0	1	0	1	0	1	1	x	0	0	x	x	0	1	x
1	0	1	1	1	1	0	0	x	0	1	x	x	1	x	1
1	1	0	0	0	0	0	0	x	1	x	1	0	x	1	x
1	1	0	1	1	1	1	0	x	0	x	0	1	x	x	1
1	1	1	0	1	1	1	1	x	0	x	0	x	0	1	x
1	1	1	1	0	0	0	0	x	1	x	1	x	1	x	1

$J_B = A$   
 $J_B = A$

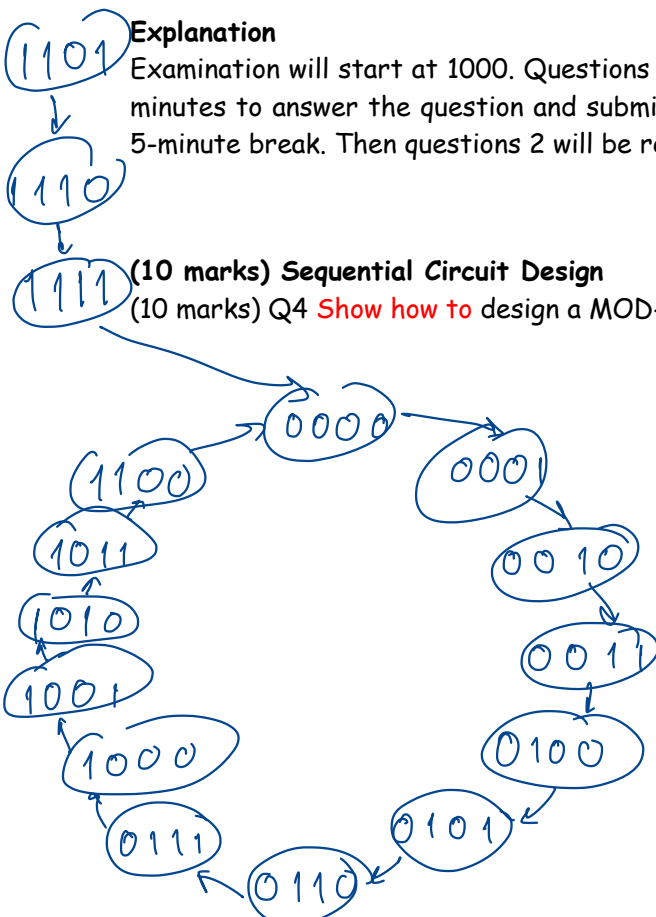 $J_A = K_A = 1$ 

$K_C$

$D_C \backslash BA$	00	01	11	10
00	X	X	X	X
01	0	0	1	0
11	X	X	X	X
10	1	0	1	0

$\swarrow$   $BA$   
 $\searrow$   $D\bar{B}\bar{A}$

$$K_C = BA + D\bar{B}\bar{A}$$

$J_C$

$D_C \backslash BA$	00	01	11	10
00	0	0	1	0
01	X	X	X	X
11	X	X	X	X
10	0	0	1	0

$\swarrow$   $BA$   
 $\searrow$   $J_C = BA$

$K_D$

$D_C \backslash BA$	00	01	11	10
00	X	X	X	X
01	X	X	X	X
11	1	0	1	0
10	0	0	0	0

$\swarrow$   $BA$   
 $\searrow$   $K_D = C\bar{B}\bar{A} + CBA$

$$J_D = CBA$$