

**Mahidol University, International College & Faculty of Engineering**  
**Department of Computer Engineering**  
**Final Examination**  
**EGCI 234: Digital Circuit Design (T2/2021-22)**

WebEx Q1 Q2

Date: 4 April 2022

Time: 2 Hours

Total Mark: 50 marks

---

**Instruction:** Answer all questions and submit to our Google Classroom

Questions **1 & 2** 25 minutes/ 5 & 9 marks (**1000-1025**) **MSI & Arithmetic Circuits**

- 5 min break -

Questions **3** 15 minutes/ 3 & 5 marks (**1030-1045**) **Flip Flops**

- 5 min break -

Questions **4** 20 minutes/ 10 marks (**1050-1110**) **Sequential Circuit Design**

- 5 min break -

Questions **5** 20 minutes/ 4 & 8 marks (**1115-1135**) **ADC & DAC**

- 5 min break -

Questions **6** 10 minutes/ 6 marks (**1140-1150**) **Digital Circuit Design**

**Explanation**


Examination will start at 1000. Questions 1 & 2 will be released via Google classroom. Students have 25 minutes to answer the question and submit to Google classroom before deadline (ie. 1025). Followed by 5-minute break. Then questions 3 will be released ..

**(14 marks) MSI & Arithmetic Circuits**

(5 marks) Q1 Show how to design a 3-bit word 2:1 MUX

$$S_0 = 0 \rightarrow I_0$$

$$S_1 = 1 \rightarrow I_1$$

 


$\therefore$  3-bit word 2:1 MUX construct the same as 1-bit word 2:1 MUX

S	$I_1$	$I_0$	O
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$$O = \bar{S}I_0 + SI_1$$

S	O
0	$I_0$
1	$I_1$

$$O = \bar{S}I_0 + SI_1$$

 

(9 marks) Q2 Show how to design a circuit that accepts  $X_{3210}$  as inputs and produces  $Y_{3210}$  as outputs (see table below).

Inouts ( $X_3X_2X_1X_0$ )	Outputs ( $Y_3Y_2Y_1Y_0$ )
0000	0011
0001	0100
0010	0101
0011	0110
0100	0111
1011	1000
1100	1001
1101	1010
1110	1011
1111	1100

From 0-4 Output = input + 3

From 11-15 Output = input - 3

$$\bar{X}_3 \bar{X}_1 \bar{X}_0 + \bar{X}_3 \bar{X}_2 X_1 X_0 + X_3 X_2 \bar{X}_1 X_0 + X_3 X_2 X_1 \bar{X}_0$$

PS	NS	$D_3$	$D_2$	$D_1$	$D_0$
0000	0011	0	0	1	1
0001	0100	0	1	0	0
0010	0101	0	1	0	1
0011	0110	0	1	1	0
0100	0111	0	1	1	1
1011	1000	1	0	0	0
1100	1001	1	0	0	1
1101	1010	1	0	1	0
1110	1011	1	0	1	1
1111	1100	1	1	0	0

$D_0 = \bar{X}_0$

$D_2 = \bar{X}_3 \bar{X}_2 X_1 + \bar{X}_3 \bar{X}_2 \bar{X}_1 X_0 + \bar{X}_3 X_2 \bar{X}_1 X_0 + X_3 X_2 X_1 X_0$

$D_3 = X_3$

0000 → 0011

0010 → 0101

0100 → 0111

1011 → 1000

(9 marks) Q2 Show how to design a circuit that accepts  $X_{3210}$  as inputs and produces  $Y_{3210}$  as outputs (see table below).

Inouts ( $X_3X_2X_1X_0$ )	Outputs ( $Y_3Y_2Y_1Y_0$ )
0000	0011
0001	0100
0010	0101
0011	0110
0100	0111
1011	1000
1100	1001
1101	1010
1110	1011
1111	1100

Input + 3 = output

