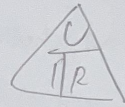


Lab 01

By
Nathan Tanaboriboon 6681224
Saharat Bhinjaren 6680208



R (ohm) 22k 10k 4.7k 1k

Forward

V_D 0.52 0.25 0.206 0.6820

bias

V_R 9.48 9.95 9.994 9.318

I_D 0.43mA 0.995mA 2.08mA 9.318mA

$$I_D = I_{total} = \frac{V_R}{R}$$

Reverse

V_D -9.994 -9.988 -9.994 -9.999

bias

V_R -0.026V -0.012V -0.006V -0.001V

I_D -1.19μA -1.24μA -1.29μA -1.02μA

