

Submitted by.....

1. For the circuit in Fig. 1, find :

- $i(0^+)$ and $v(0^+)$.
- $di(0^+)/dt$ and $dv(0^+)/dt$.
- $i(\infty)$ and $v(\infty)$.

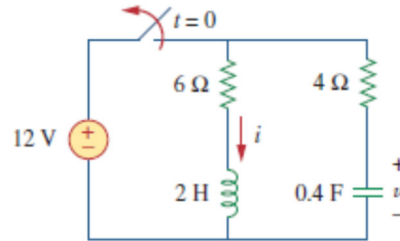


Fig. 1.

Ans

- $i(0^+) = 2A$; $v(0^+) = 12V$
- $\frac{di(0^+)}{dt} = -4A/s$; $\frac{dv(0^+)}{dt} = -5V/s$
- $i(\infty) = 0A$; $v(\infty) = 0V$

2 For the circuit in Fig. 2, find :

- $v(0^+)$ and $i(0^+)$.
- $dv(0^+)/dt$ and $di(0^+)/dt$.
- $v(\infty)$ and $i(\infty)$.

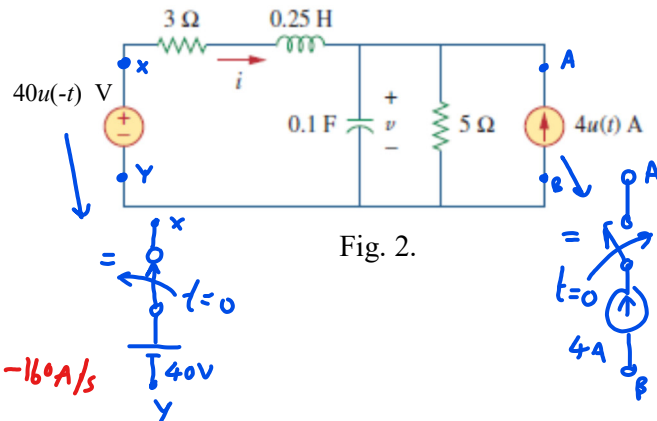
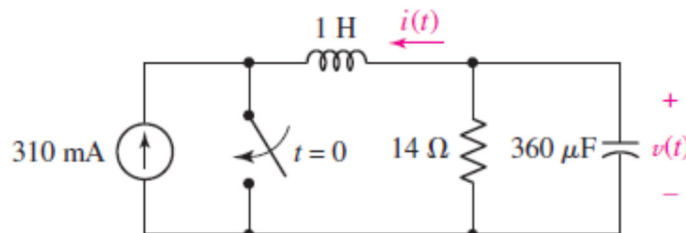


Fig. 2.

Ans

- $v(0^+) = 25V$; $i(0^+) = 5A$
- $\frac{dv(0^+)}{dt} = 40V/s$; $\frac{di(0^+)}{dt} = -16A/s$

3. Obtain expressions for the current $i(t)$ and voltage $v(t)$ as labeled in the circuit of Fig. 3. which are valid for all $t > 0$.

Ans This problem is the 2nd-order $\rightarrow$ skip But $i_L(0^-) = i_L(0^+) = -310mA$
 $v_C(0^-) = v_C(0^+) = 4.34V$

Submitted by.....

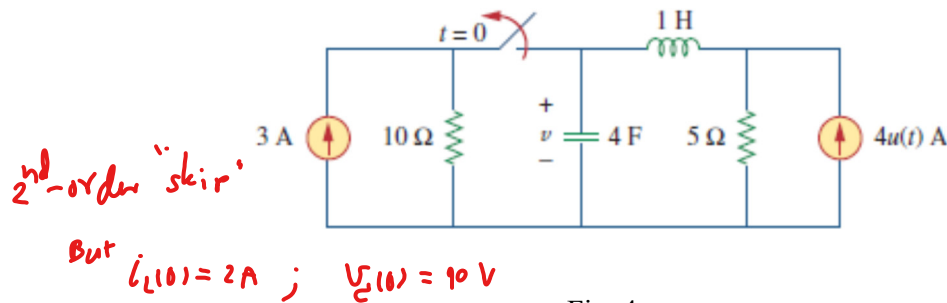
4. Find $v(t)$ for $t > 0$ in the circuit of Fig. 4.

Fig. 4.

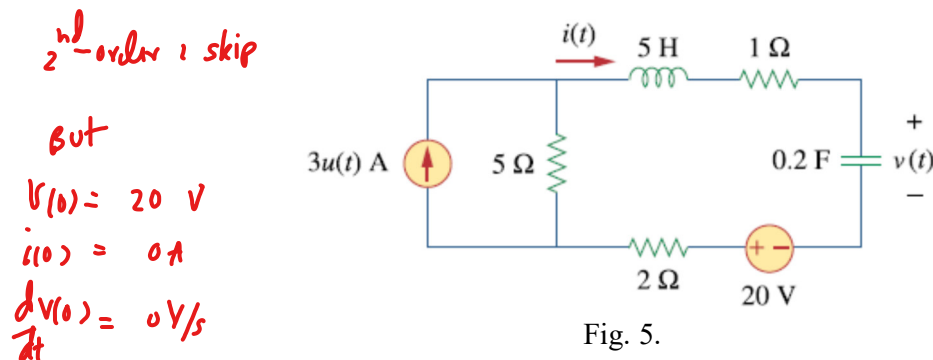
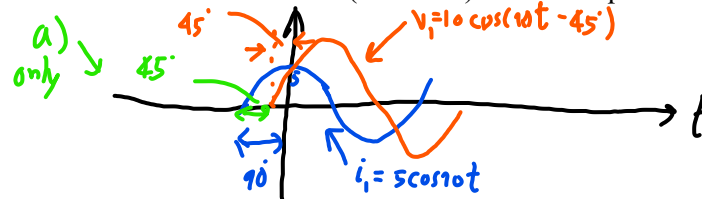
5. Obtain $v(t)$ and $i(t)$ for $t > 0$ in the circuit of Fig. 5.

Fig. 5.

6. Determine the angle by which v_1 leads i_1 if $v_1 = 10 \cos(10t - 45^\circ)$ and i_1 is equal to

- (a) $5 \cos 10t = 45^\circ$
- (b) $5 \cos(10t - 80^\circ)$
- (c) $5 \cos(10t - 40^\circ)$
- (d) $5 \cos(10t + 40^\circ)$
- (e) $5 \sin(10t - 19^\circ)$.

7. In the circuit of Fig.7 , which is shown in the phasor (frequency) domain, I_{10} is determined to be $2 \angle 42^\circ$ mA. If $V = 40 \angle 132^\circ$ mV:

- (a) what is the likely type of element connected to the right of the $10\ \Omega$ resistor and
- (b) what is its value, assuming the voltage source operates at a frequency of 1000 rad/s ?

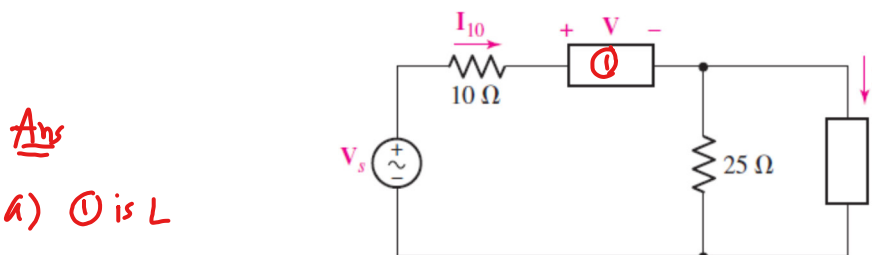


Fig. 7.

Submitted by.....

8. For the RLC circuit of Fig. 7, determine $\mathbf{I}_s$ and $i_s(t)$ if both sources operate at $\omega = 2 \text{ rad/s}$, and $\mathbf{I}_C = 2\angle 28^\circ \text{ A}$.

Ans

$$\mathbf{I}_s = 1.5\angle -62^\circ$$

$$i_s(t) = 1.5 \cos(2t - 62^\circ)$$

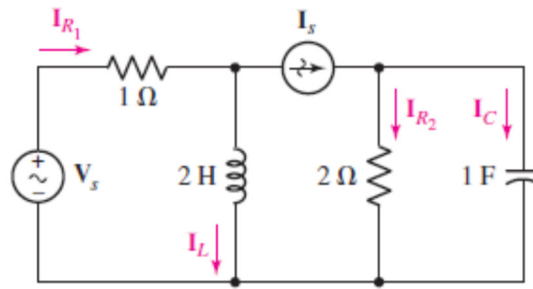


Fig. 8.

9. Obtain expressions for the time - domain currents $i_1(t)$ and $i_2(t)$ in the circuit given as Fig. 8.

Ans

$$i_1(t) = 1.24 \cos[1000t + 29.7^\circ]$$

$$i_2(t) = 2.77 \cos[1000t + 56.3^\circ]$$

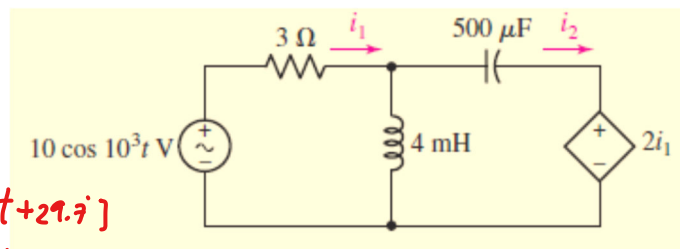


Fig. 9.

10. Calculate the complex power delivered to each passive component of the circuit shown in Fig. 10, and determine the power factor of the source.

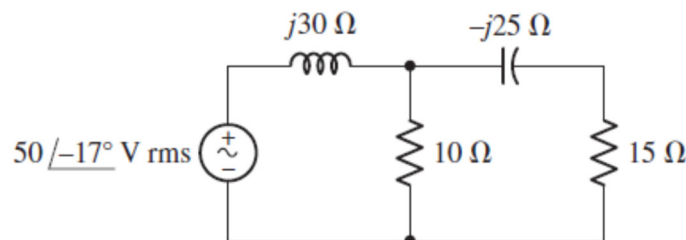


Fig. 10.

Ans

complex power

$$\mathbf{S}_{j30\Omega} = 88.40\angle 90^\circ \text{ VA (OR } Q = 88.40 \text{ VAR)}$$

$$\mathbf{S}_{10\Omega} = 20\angle 0^\circ \text{ VA (OR } P_{10\Omega} = 20 \text{ watt)}$$

$$\mathbf{S}_{-j25\Omega} = 5.865\angle -90^\circ \text{ VA (OR } Q = -5.865 \text{ VAR)}$$

$$\mathbf{S}_{15\Omega} = 3.517\angle 0^\circ \text{ VA (OR } P_{15\Omega} = 3.517 \text{ watt)}$$

$$\mathbf{S}_{\text{source}} = 85.85\angle 74.05^\circ \text{ VA}$$

$$= 23.57 + j82.54 \text{ VA}$$

$$\text{p.f.} = \cos(74.05^\circ)$$

$$= 0.274 \text{ (lagging)}$$